

Quiz # One

Student Name: _____ student ID: _____


Q1. If two adjacent 1s are detected in the input, the output is set to high input combinations will be

- a) 1100
- b) 0011
- c) 0101
- d) 1010

Q2. On solving the expression $Y = (a+c+d).(a+c+d').(a+c'+d).(a+d')$, we get the value of Y to be:

- a) $a'c' + a'cd' + a'd$
- b) a'
- c) $a'c'$
- d) a

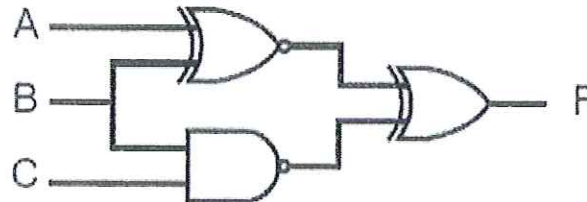Q3. Which of the following expression represents the given circuit?



- a) $F = (A \oplus B)' \oplus (B' + C')$
- b) $F = B(A \oplus C)' + AB'$
- c) $F = (A \oplus B) + C'$
- d) $F = (A' \oplus B') \oplus (B' + C')$

Q4. The number of bits needed to address 4K memory is

- a) 12
- b) 6
- c) 8
- d) 16

Q5. De Morgan's theorems states that $(X+Y)' = X'.Y'$. Simply stated, this means that logically there is no difference between:

- a) a NOR and a NAND gate with inverted inputs
- b) a NOR and an AND gate with inverted inputs
- c) an AND and a NOR gate with inverted inputs
- d) a NAND and an OR gate with inverted inputs

Q6. How many 1s are there in the binary representation of $15 \times 256 + 5 \times 16 + 3$?

- a) 10
- b) 9
- c) 8

d) 11


Q7. The Boolean expression $A'B + AB' + AB$ is equivalent to

- a) $A + B$
- b) $A.B$
- c) $(A + B)'$
- d) $A'.B$

Q8. Which of the following combinations of gates does not allow the implementation of an arbitrary Boolean function?

- a) OR gates and exclusive – OR gates only
- b) NAND gates only
- c) OR gates and inverters gates only
- d) OR gates and NAND gates.

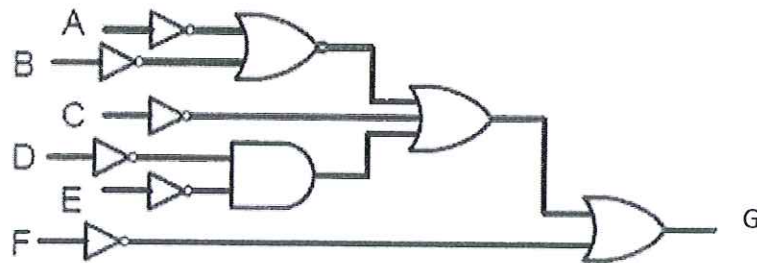Q9. Which of the following expression represents the given circuit?



- a) $G = F' + D'E' + C' + A'B'$
- b) $G = F' + D'E' + C' + AB$
- c) $G = F' + D'E' + C' + AB$
- d) $G = F' + DE + C' + A'B'$

Q10. The simplification of the Boolean expression $A'B.C'.A.B'.C$ is

- a) A
- b) 1
- c) 0
- d) BC

Q11. The Boolean expression $(C \oplus D)(B + D + C)$ may be simplified as

- a) CB
- b) $CD + C'D'$
- c) $B + C \oplus D$
- d) $B' + CD$

Q12. Which of the following sets represents a universal logic family?

- a) XOR
- b) AND
- c) NAND
- d) None of the above