

Question #1 (25 points)

(A) We have the following numbers stored in the computer. What is the decimal value presented if the number is stored as: (12 points)

- a) BCD 2421 b) BCD excess 3
c) Binary unsigned d) Binary Signed

- 1) 1000 0111 2) 0101 0100 3) 1100 0110

(B) Reduce the expression below to a minimum sum of products form using switching algebra. Show each step. (5 points)

$$G = (a+b)(a+c') + ab'$$

(C) Given the function of question 1-(B): (8 points)

$$G = (a+b)(a+c') + ab'$$

- Show a block diagram for two level implementation of the minimized function using AND and OR gates.
- Show a block diagram for an implementation of G after minimization using only two input NANDs

Question #2 (24 points)

Given the following functions:

$$F(w,x,y,z) = \sum m(0, 4, 5, 6, 7, 12, 15)$$

$$G(w,x,y,z) = \sum m(1, 3, 12, 13, 14, 15)$$

- Implement them using PLA that has 4-inputs 3-outputs and 2 eight AND Gates.
 - Implement them using 3-input 8-output decoders with two enables, EN1 and EN2'.
 - Implement them using a ROM that has four inputs and three outputs.
- Be sure to label the inputs and outputs of each design.

Question #3 (24 points)

Design a network that computes the residue mod 7 of an integer in the range 0 to 15. Minimize the output to permit sharing then implement the system.

Question #4 (27 points)

(A) Obtain the state description of a sequential system having the following time behavior: (12 points)


Input: $x(t) \in \{0,1\}$

Output: $z(t) \in \{0,1\}$

$$z(t) = \begin{cases} 1 & \text{if } x(t-2,t) = 1010 \\ 0 & \text{otherwise} \end{cases}$$

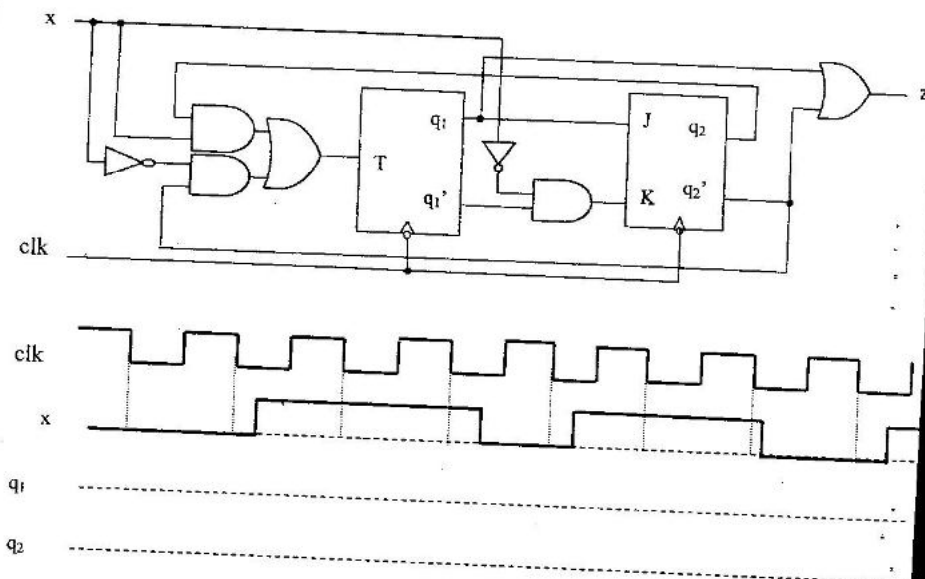(B) Given the following sequential network: (15 points)

- Obtain the high level description (i.e., input, output, states, state table and state diagram)
- Complete the timing diagram (i.e., draw the timing diagram for q_1 and for q_2)



Best of Luck ☺