



Answer the following questions: Clarify your answer, start each problem in a new page.
Label your signal lines in each and every Design and Table.

Question 1: (9 points)

- a) Using the version of Hamming code shown, Code the data "1001"
- $$a1 = a3 \oplus a5 \oplus a7$$
- $$a2 = a3 \oplus a6 \oplus a7$$
- $$a4 = a5 \oplus a6 \oplus a7$$
- b) If the word "1101101", was received after being coded with Hamming code, what word was sent (assuming single error).
- c) Given the two binary numbers 10010101 and 01110011,
Show the decimal equivalent of each of the numbers if they are interpreted as:
- BCD Excess3
 - BCD 8421
 - Signed number
 - Unsigned number

Question 2: (9 points)

- a) Show the Truth Table for a system that has four inputs, a, b, c and d , and two outputs, f and g . The first two inputs (a, b) represent one binary number (in the range 0 to 3) and the last two (c, d) represent another number in the range 1 to 3. The output, f and g represent the magnitude of the difference of the two binary numbers inputs ($|ab - cd|$).
- b) Reduce the following expression to a minimum Sum of products, show each algebraic step.
- $$F(w, x, y, z) = x'z' + x'yz' + xy'z + xyz + wx'z$$
- c) Manipulate the following to sum of product expression
- $$F = (b' + c)(a' + c + d')(c' + d)(a + c' + d')$$

Question 3: (9 points)

- a) Given the function, F , written in the following page, show a block diagram for the implementation of the function using, only, two-input NAND gates (any number of them). Assume all variables are available, both complemented and uncomplemented.

$$F = abc + ac'd'e' + a'd'e + ce + cd$$

(helping note: Manipulate the expression to obtain terms containing two literals or less, then draw schematic of the function).

- b) Find all minimum Sum of products expressions for the following functions (use K-Map):
(three solutions)

$$G(a, b, c, d, e) = \sum m(0, 3, 5, 7, 12, 13, 14, 15, 19, 20, 21, 22, 23, 25, 26, 29, 30)$$

Question 4: (12 points)

Consider the following three function:

$$F = \sum m(1, 2, 3, 5, 6, 7, 8, 10, 11, 15)$$

$$G = \sum m(3, 4, 6, 8, 12, 14, 15)$$

$$H = \sum m(1, 3, 4, 5, 6, 7, 8, 15)$$


- a) Implement them using ROM gate arrays, be sure to label the inputs and the outputs.
- b) Given the shown decoder, with active low outputs, active low enable, implement the given functions. Use three NAND gates and at most five of the shown decoder.
Extra 5 points credit: Show a diagram that uses, only, three eight-input NAND gates and four of this decoder.

4 decoder

EN'	A	B	0	1	2	3
0	1	X	X	1	1	1
1	0	0	0	0	1	1
2	0	0	1	1	0	1
3	0	1	0	1	1	0
	0	1	1	1	1	0

Question 5: (9 points)

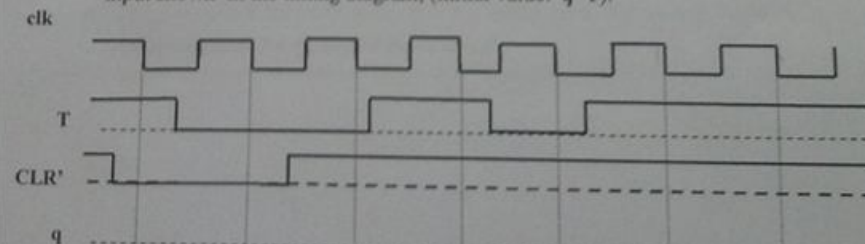- a) Given a T flip flop with an active low clear (CLR'). Show the Flip Flop output for the input shown in the timing diagram, (initial value: $q=1$).



- b) We have a new type of a Flip Flop, with inputs A and B , if $A=0$ then $Q^*=QB$,
If $A=1$ then $Q^*=Q'B$.

- Show a state diagram for this Flip Flop
- Write an equation for Q^* in terms of A , B and Q .


Question 6: (10 points)

A system that has two inputs ($x, y \in \{a, b\}$) and one output ($z \in \{0, 1\}$). The output z is one when x equals to y for at least three consecutive clock cycles, and is zero, otherwise.

- Describe the system
- State the system Model
- Show the transition and the output functions in a state table
- Draw the state diagram

Question 7: (12 points)

Given the following circuit:

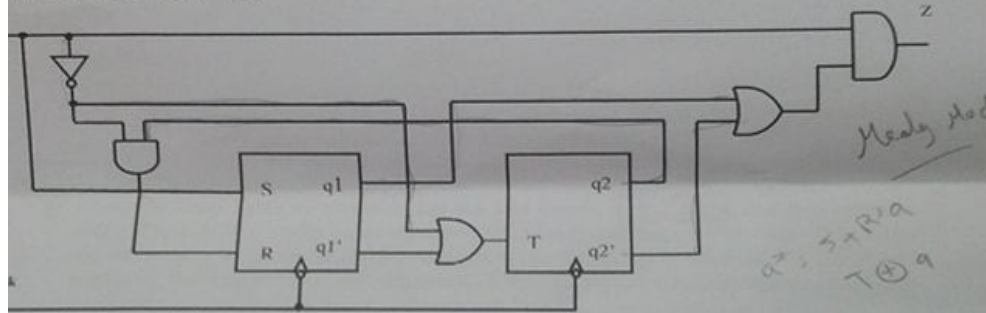

- State the design model
- Build the state table
- Given the initial state (00) and following values for x : 001100110, build the time Trace (behavior) table for q_1 , q_2 and the output z .

☺ Best of LUCK ☺