



Question 1:

Knowing that, the data are manipulated in a computer that stores two decimal digits, find the solution of the following **in binary**, then convert the result into **decimal value**.

- $00110110 - 11000110$ *2's complement* comment on the result
- $10110011 + 00101011$ comment on the result
- The **Excess-3 BCD** of the decimal digits 59. *10001100*
- The **signed binary number** for the decimal number -59. *1111011*
- The **2's complement** of the decimal number -62. *1100110*

Question 2:

Find all the minimum expressions in both **Sum of Products and Product of Sums forms** for the following:

- $F(a,b,c,d) = \sum m(3,4,9,13,14,15) + \sum d(2,5,10,12)$, using *k-map* ✓ *$AB + AC + BC + \bar{A}\bar{B}$*
- $H(w,x,y,z) = wx + w'xz + xyz + wxy' + w'xz' + w'y$, using *Algebraic rules* *$x + xyZ + \bar{w}$*

Question 3:

Assume all input are available both uncomplemented and complemented, draw the Implementation of the logical function:

$$G(a,b,c,d) = a'b'd' + bde' + bc'd + a'ce$$

- In a two-level schematic using **NAND** gates of any size,
- In a two-level schematic using **NOR** gates of any size,
- Using tow-input **NAND** gates (none of which may be used as a NOT)

Question 4:

Design a **synchronous counter** that go through the sequence 13, 7, 8, 2, 15, 9, 14; using **T flip flop**.

- Find the flip flops input equations
- Show the state diagram for the counter indicating what happens if the system, initially, is in one of the **unused states**.

Question 5:

A counter with two **D FFs**, **A** and **B** and control line **x**. If $x = 0$, it counts 0, 3, 1 and repeat; if $x = 1$, it counts 1, 2, 3 and saturate (i.e., 1 2 3 3 3...).

- Assume that **x** changes only when it is in state 1 or 3, calculate the Flip Flop inputs
- Implement the counter using **AND**, **OR** and **NOT** gates.
- Show if it is a self started system, illustrate your answer with the state diagram.

Question 6:

Design, minimize and implement a combinational circuit that convert from the *BCD* 2421 code to the 2-of-5 code. The following is the truth table for them.
(Consider the do not cares!!)

2421 Code	2 of 5 Code	2421 Code	2 of 5 Code
0000	11000	1011	01010
0001	10100	1100	01001
0010	10010	1101	00110
0011	10001	1110	00101
0100	01100	1111	00011

Question 7:

Design the solution for sequential system specified by the following state table and state assignment using a *D* flip flop for q_1 and *JK* flip flop for q_2 .

- Find the flip flop input equations
- Find system output equation
- Show a block diagram of the system using *AND*, *OR* and *NOT* gates.

State Table

q	q^*		z
	$x=0$	$x=1$	
A	0C	0B	1
B	0C	1A	1
C	1A	0C	0

State Assignment

q	q_1	q_2
A	1	1
B	0	1
C	1	0