



Solve here: (c): Minimize each function

v=

w=

x=

y=

z=

(B) Use switching Algebra rules to reduce the following expression to a minimum Sum of products and a minimum Product of sums, show each step.

$$G = wx + x'y + wyz + wxz' + wyz'$$

Question 3: (6 points)

Given the function, (assume all variables are available, both complemented and uncomplemented)

$$F = a'b' + a'c + ab'$$



- Show a block diagram for a two level implementation of  $F$  using *And* and *OR* gates
- Show a block diagram for an implementation of  $F$  using Only, NAND gates
- Expand  $F$  to sum of minterms, eliminate any duplications.

**Question 4: (8 points)**

Find the minimum Sum of products, and the minimum Product of sums for the following functions ((that is, using K-map, circle the terms on the map and write the algebraic expressions):

- a)  $F(A,B,C,D,E) = \Sigma m(0,1,5,6,7,8,9,14,17,20,21,22,23,25,28,29,30)$   
 b)  $G(WX,Y,Z) = \Sigma m(4,6,11,12,13) + \Sigma d(3,5,7,9,10,15)$


Solution (a)

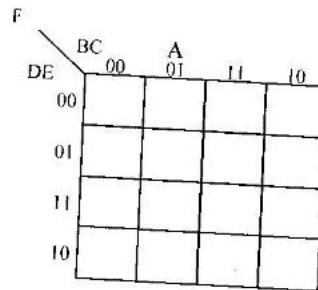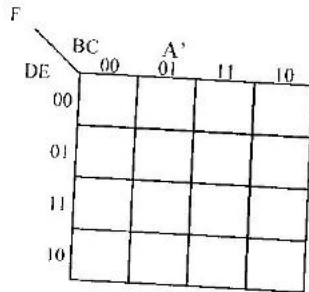

F=

Solution (b):
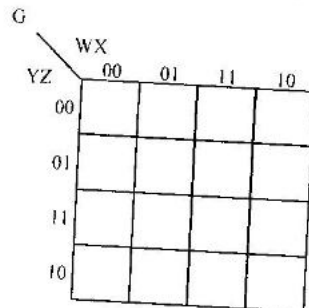
$$G(WX,Y,Z) = \Sigma m(4,6,11,12,13) + \Sigma d(3,5,7,9,10,15)$$



G=

**Question 5: (12 points)**

It is required to build a converter that convert from *BCD2-of-5* code to *BCD5421* (the two codes are shown below)

Decimal	BCD 5421	BCD 2-of-5
0	0000	11000
1	0001	10100
2	0010	10010
3	0011	10001
4	0100	01100
5	1000	01010
6	1001	01001
7	1010	00110
8	1011	00101
9	1100	00011

All other combinations of input bits never occur



- a) Build the truth table for the *BCD 2-of-5* (five functions v,w,x,y,z) from the *BCD 5421* (four inputs a,b,c,d)  
 b) Use k-map to minimize each of the five functions v, w, x, y, z.  
 c) Implement the converter using Programmable Array Logic (PAL) with 12 *AND* gates and five 4-input *OR* gates, show the terms and its sums.

Solve here

(a) Truth table

a	B	c	d	v	w	x	y	z

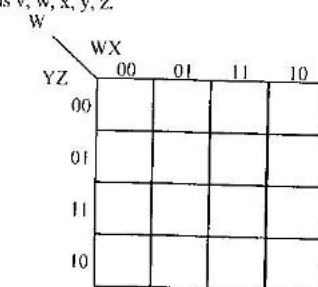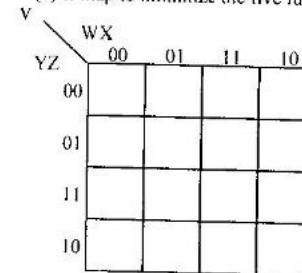(b) k-map to minimize the five functions v, w, x, y, z.



v=

x YZ	WX			
	00	01	11	10
00				
01				
11				
10				

x=

w=


y YZ	WX			
	00	01	11	10
00				
01				
11				
10				

y=

Z YZ	WX			
	00	01	11	10
00				
01				
11				
10				

z=

(c) Programmable Array Logic (PAL) implementation

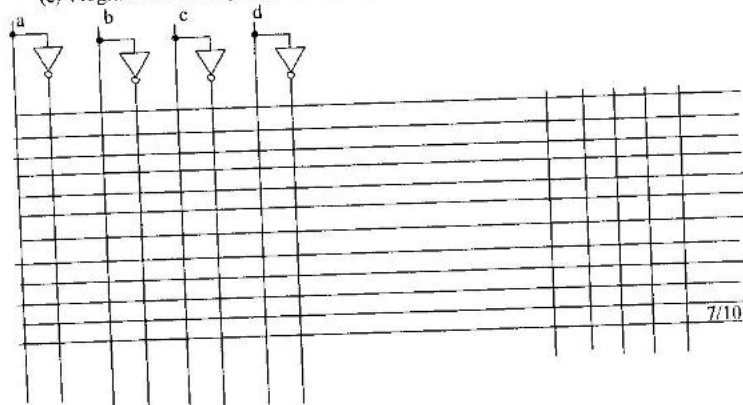

Question 6: (10 points)

A system has one input ( $x \in \{a, b\}$ ) and one output ( $z \in \{0, 1\}$ ). The output  $z$  is one iff the input ( $x$ ) had been the same for three consecutive clock cycles, otherwise,  $z$  is zero. Assume  $x = a$  as an initial state.

- a- Describe the system, including its initial state
- b- State the system Model
- c- Show the transition and the output functions in a state table
- d- Draw the state diagram

Solve here

- a) Describe the system


b) System Model is

c) State Table

d) State Diagram

**Question 7: (10 points)**

Given the following circuit:

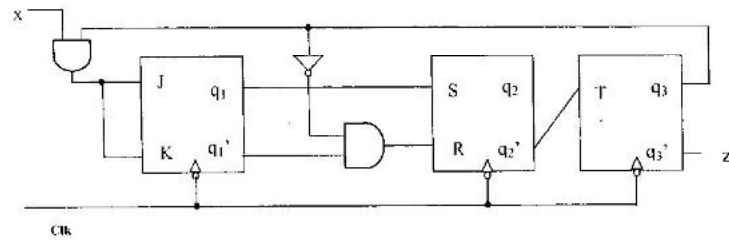

- State the design model
- Build the state table
- Assuming the initial state for  $q_1, q_2, q_3$  to be (000) complete the given timing diagram for the circuit.


[Solve Here](#)

a) Design model is

c) State Table

Q1	Q2	Q3		

c) Timing diagram for the circuit:

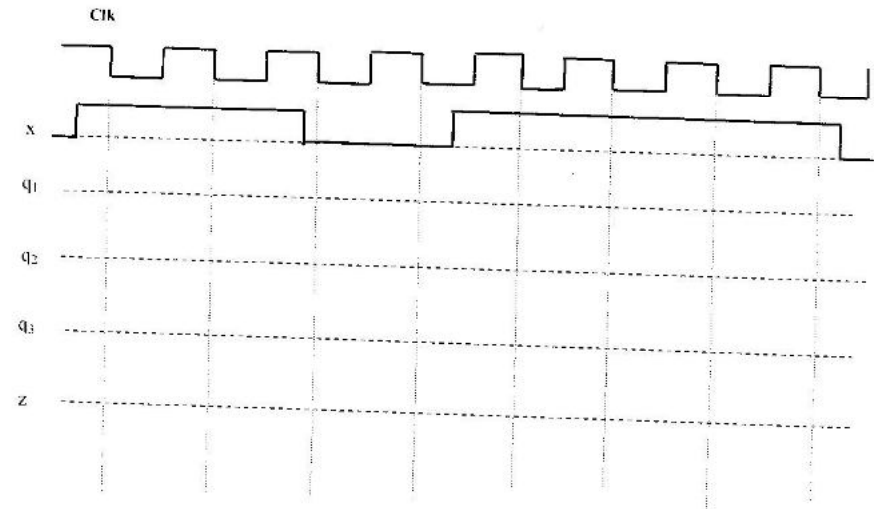

☺ Best Of LUCK ☺