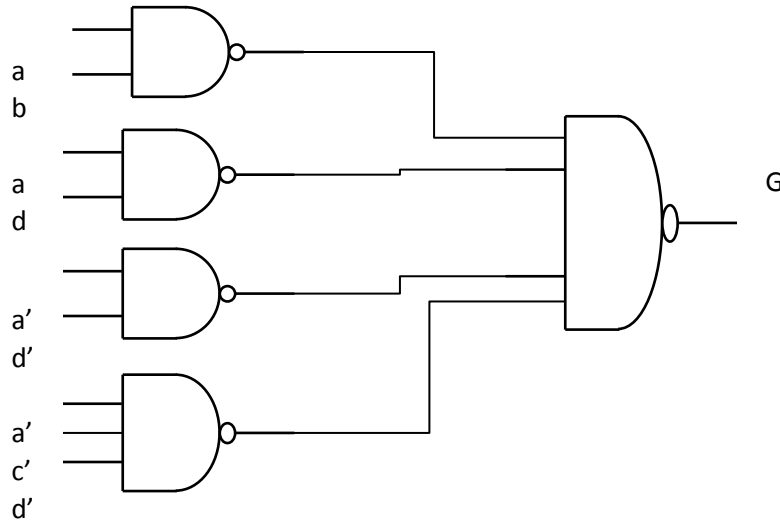


Quiz #3

Q1. Assume all input are available both uncomplemented and complemented, show a two-level implementation of:


$$G(a,b,c,d) = ab + ad + a'b' + a'c'd' = (a'+b+d)(a+b'+c')(a+b'+d')$$

a- Using Nand gates of any size




b- Using nor gates of any size

$$G = (a'+b+d)(a+b'+c')(a+b'+d')$$

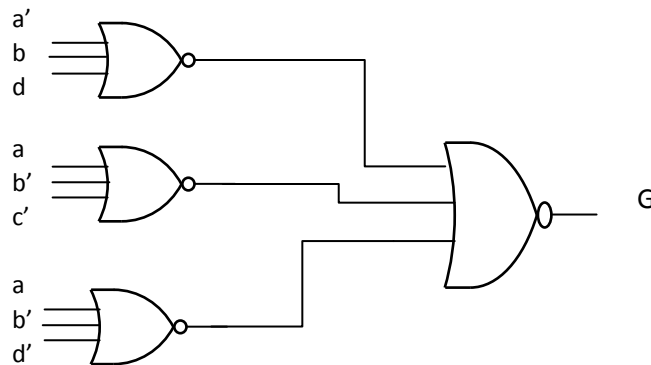

c- Using two-input NAND gates (none of which may be used as a NOT)
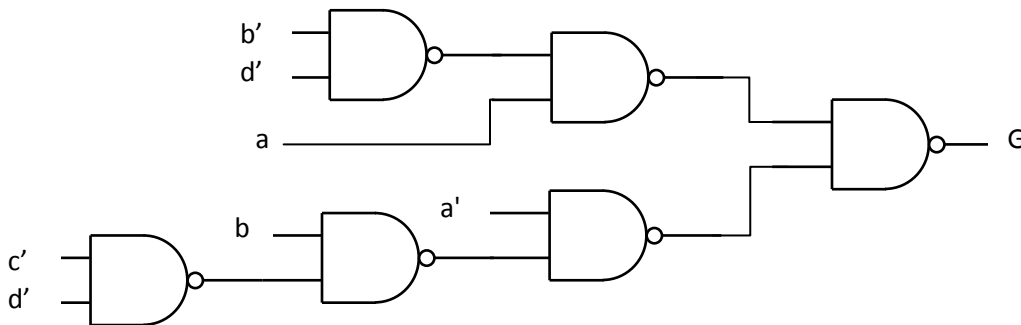
$$g = ab + ad + a'b' + a'c'd' = a(b+d) + a'(b'+c'd')$$



Q2. Given the following truth table

<i>x</i>	<i>y</i>	<i>z</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

a- Write the sum of minterm function in numeric form

$$F = \sum m(1,2,4,6,7)$$

b- Write the sum of minterm function in Algebraic form

$$F = x'y'z + x'yz' + xy'z' + xyz' + xyz$$

c- Find the minimum sum of products expression

$$\begin{aligned} F &= x'y'z + x'yz' + xy'z' + xyz' + xyz = x'y'z + x'yz' + xyz' + xz'(y' + y) \\ &= x'y'z + yx'z' + xyz' + xz' = x(z' + yz) + z'(x + yx') + x'y'z = xz' + xy + xz' + yz' + x'y'z \\ &= xz' + xy + yz' + x'y'z \end{aligned}$$

d- Find the minimum product of sum expression

$$\begin{aligned} F &= xz' + xy + yz' + x'y'z = z'(x+y) + x'y'z + xy \\ &= (z' + x'y')(z + x + y) + xy = (xy + (z' + x'y'))(xy + (z + x + y)) = ((x+y')(x'+y) + z')(z + x + y) \\ &= (x+y' + z')(x' + y + z')(z + x + y) \end{aligned}$$

Q3. Given the following sequence of 6 state: 4 7 2 0 3 1

a) Design a counter to generate the sequence using *T Flip Flop*.

b) Show the state diagram indicating what happens if it, initially, is in one of the unused states.

- c) Propose a solution for the problems caused by the unused states.
d) Design the solution you proposed in 'c'

Sol

a)

$Q2$	$Q1$	$Q0$	$Q2^*$	$Q1^*$	$Q0^*$	$T2$	$T1$	$T0$
0	0	0	0	1	1	0	1	1
0	0	1	1	0	0	1	0	1
0	1	0	0	0	0	0	1	0
0	1	1	0	0	1	0	1	0
1	0	0	1	1	1	0	1	1
1	0	1	X	X	X	X	X	X
1	1	0	X	X	X	X	X	X
1	1	1	0	1	0	1	0	1

$$T0 = \Sigma M(0, 1, 4, 7) + \Sigma D(5, 6)$$

$$T1 = \Sigma M(0, 2, 3, 4) + \Sigma D(5, 6)$$

$$T2 = \Sigma M(1, 7) + \Sigma D(5, 6)$$

	00	01	11	10
0	1		x	1
1	1		1	x

$$T0 = Q2 + Q1'$$

$$T1 = \Sigma M(0, 2, 3, 4) + \Sigma D(5, 6)$$

	00	01	11	10
0	1	1	x	1
1		1		x

$$T1 = Q0' + Q2'Q1$$

$$T2 = \Sigma M(1, 7) + \Sigma D(5, 6)$$

	00	01	11	10
0			x	
1	1		1	x

$$T2 = Q1Q2/q2q0 + Q1'Q0$$

$$T0 = Q2 + Q1'$$


$$T1 = Q0' + Q2'Q1$$

$$T2 = Q1Q2/q2q0 + Q1'Q0$$

	T2	T1	T0	
101	1/1	0	1	000/000 used states
110	1/0	1	1	001/101 USED 1, unused 5

b) State Diagram

4 7 2 0 3 1

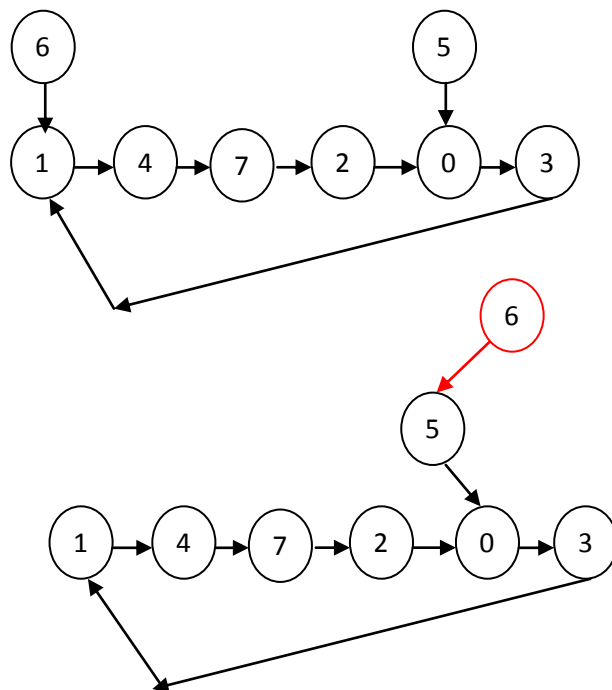

c) THE FIRST SOLUTION IS A SELF STATED DESIGN SOLUTION
OR IF YOU HAVE TO USE THE SECOND SOLUTION THEN YOU must REDESIGN IT.
It SHOULD BE REDESIGNED WITH THE STATE '110' AS A USED STATE

d) design for the same sequence with state '110' → '001'

$Q2$	$Q1$	$Q0$	$Q2^*$	$Q1^*$	$Q0^*$	$T2$	$T1$	$T0$
0	0	0	0	1	1	0	1	1
0	0	1	1	0	0	1	0	1
0	1	0	0	0	0	0	1	0
0	1	1	0	0	1	0	1	0
1	0	0	1	1	1	0	1	1
1	0	1	x	x	x	x	x	x
1	1	0	0	0	1	1	1	1
1	1	1	0	1	0	1	0	1

$$T0 = \Sigma M(0, 1, 4, 6, 7) + \Sigma D(5)$$

$$T1 = \Sigma M(0, 2, 3, 4, 6) + \Sigma D(5)$$

$$T2 = \Sigma M(1, 6, 7) + \Sigma D(5)$$

$T0$

	00	01	11	10
0	1		1	1
1	1		1	x

$$T0 = Q2 + Q1'$$

$T1$

	00	01	11	10
0	1	1	1	1
1		1		x

$$T1 = Q0' + Q2'Q1$$

$T2$

	00	01	11	10
0			1	
1	1		1	x

$$T2 = Q1Q2 + Q1'Q0$$

$$T0 = Q2 + Q1'$$

$$T1 = Q0' + Q2'Q1$$

$$T2 = Q1Q2 + Q1'Q0$$

Check self starting

	$T2$	$T1$	$T0$	
101	1	0	1	000 USED 0

The state diagram

