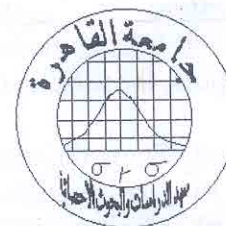




Institute of Statistical Studies and Research
Department of Computer and Information Sciences
 Digital Logic – CS504
 January 2013
 Time permitted: Three Hours



Question 1: (8 points)

- a) Using the version of Hamming code shown, Code the data “1011”

$$a1 = a3 \oplus a5 \oplus a7$$

$$a2 = a3 \oplus a6 \oplus a7$$

$$a4 = a5 \oplus a6 \oplus a7$$

- b) If the word “1010101”, was received after being coded with Hamming code, what word was sent (assuming single error).

- c) We have a computer that can store three decimal digits (12 bits). How are the following numbers stored, using the specified code/form?:

- (i) BCD Excess3 (157) (ii) BCD 8421 (91) (iii) BCD 5421 (238)

- (iv) 2's Complement (-98) (v) Signed integer (-124)

Question 2: (10 points)

- a) Show the Truth Table for a system that has four inputs, a, b, c and d , and one output, f . The first two inputs (a, b) represent one binary number (in the range 0 to 3) and the last two (c, d) represent another number in the range 1 to 3. The output, f , is to be one, iff, the second number is larger than the first.

- b) Reduce the following expression to a minimum Sum of products and a minimum Product of sums, **show** each step.

$$F(w, x, y, z) = x'y'z + w'xz + wxyz' + wxz + w'xyz$$

- c) Manipulate the following to sum of product expression

$$F(a, b, c, d) = (a+b+c+d')(b+c+d')(b'+c')$$

Question 3: (9 points)

Given the function, [assume all variables are available, both complemented and uncomplemented]

$$F = b'c'd' + bd + acd + abc$$

- a) Show a block diagram for a two level implementation of F using *And* and *OR* gates
 b) Show a block diagram for an implementation of F using, Only, two-input NAND gates.
 c) Expand F to sum of minterms, write it in numeric form and eliminate any duplications

Question 4: (9 points)

Find the minimum Sum of products, and the minimum Product of sums for the following functions (use K-Map):

a) $F = Bc'd' + cd + bc'd + abc + bd$

b) $G = \Sigma m(3, 4, 9, 13, 14, 15) + \Sigma d(2, 5, 10, 12)$

Question 5: (12 points)

A 1-bit full subtractor that has three inputs, a borrow B_{in} , x and y , and produces Two outputs, the difference D ($D = x - y - B_{in}$) and the new borrow B_{out} .

- Show the truth table for the full subtractor
- Use the truth table to find the expressions for D and B_{out}
- Minimize and implement the subtractor using Programmable Logic Array with five AND gates, **show the shared terms**.
- Implement the subtractor using 3-8 active low decoder with one active low enable; and two OR gates.

Question 6: (12 points)

Consider the following two function:

$$F(a, b, c, d) = \sum m(1, 2, 3, 5, 6, 7, 11, 15)$$

$$G(a, b, c, d) = \sum m(1, 2, 3, 6, 11, 13, 15)$$

- Implement them using PLA gate arrays with 7 terms, show the shared terms and be sure to label the inputs and the outputs, full credit if you use 6 or less terms.
- Given the shown decoder, with active low outputs, active low enable, implement the given functions. Use two 8-input $NAND$ gates and **at most four** of the shown decoder.

	EN'	A	B	0	1	2	3
A	1	X	X	1	1	1	1
B	0	0	0	0	1	1	1
EN'	0	0	1	1	0	1	1
	0	1	0	1	1	0	1
	0	1	1	1	1	1	0

Question 7: (10 points)

A system has two inputs ($x, y \in \{a, b\}$) and one output ($z \in \{0, 1\}$). The output z is one when x has been different from y for at least two consecutive clock cycles, and is zero, otherwise.

- Describe the system
- State the system Model
- Show the transition and the output functions in a state table
- Draw the state diagram

☺ GOOD LUCK