

Answer the following questions: *Clarify your answer, start each problem in a new page. Label your signal lines in each and every Design and Table.*

Question 1: (7 points)

- Using the version of Hamming code shown, Code the data "1101"
 $a1 = a3 \oplus a5 \oplus a7$
 $a2 = a3 \oplus a6 \oplus a7$
 $a4 = a5 \oplus a6 \oplus a7$
- If the word "1101101", was received after being coded with Hamming code, what word was sent (assuming single error).
- We have a computer that can store 3 decimal digits, How are the following numbers stored, using the specified code/form:
 (i) BCD Excess3(56) (ii) BCD 8421(71) (iii) BCD 5421(65)
 (iv) 2's Complement(-47) (v) Signed integer(-124)

Question 2: (7 points)

- Show the Truth Table for a system that has four inputs, a, b, c and d , and one output, f . The first two inputs (a, b) represent one binary number (in the range 0 to 3) and the last two (c, d) represent another number in the range 1 to 3. The output, f , is to be one, iff, the second number is at least two larger than the first.
- Reduce the following expression to a minimum Sum of products and a minimum Product of sums, show each step.

$$F = x'y'z + x'yz + xy'z + xyz$$

Question 3: (7 points)

Given the function, [assume all variables are available, both complemented and uncomplemented]

$$F = abc' + ad + bd'$$

- Show a block diagram for a two level implementation of F using *And* and *OR* gates
- Show a block diagram for an implementation of F using Only, *NAND* gates
- Expand F to sum of minterms, eliminate any duplications

Question 4: (7 points)

Find the minimum Sum of products, and the minimum Product of sums for the following functions (use K-Map):

- $F = Bc'd' + cd + bc'd + abc + bd$
- $G = \sum m(0, 2, 3, 6, 8, 11, 14) + \sum d(1, 4, 5, 13, 15)$

Question 5: (10 points)

A 1-bit full subtractor that has three inputs, a borrow B_{in} , x and y , and produces Two outputs, the difference D ($D = x - y - B_{in}$) and the new borrow B_{out} .

- Show the truth table for the full subtractor
- Use the truth table to find the expressions for D and B_{out}
- Implement the subtractor using Programmable Logic Array with five *AND* gates, show the shared terms.
- Minimize and implement the subtractor using 3-8 active low decoder with one active low enable; and two *OR* gates.

Question 6: (8 points)

Show the truth table and Design, using *AND*, *OR* and *NOT*, a priority encoder with seven active low inputs, $1', 2', \dots, 7'$ and three active high outputs, CBA that indicate which is the highest priority line active. Input $7'$ is the highest and $1'$ is the lowest. If none of the inputs are active, the output is 000.


Question 7: (12 points)

A system that has two inputs ($x, y \in \{a, b\}$) and one output ($z \in \{0, 1\}$). the output z is one when x differs from y for at least three consecutive clock cycles, and is zero, otherwise.

- Describe the system
- State the system Model
- Show the transition and the output functions in a state table
- Draw the state diagram


Question 8: (12 points)

Given the following circuit:

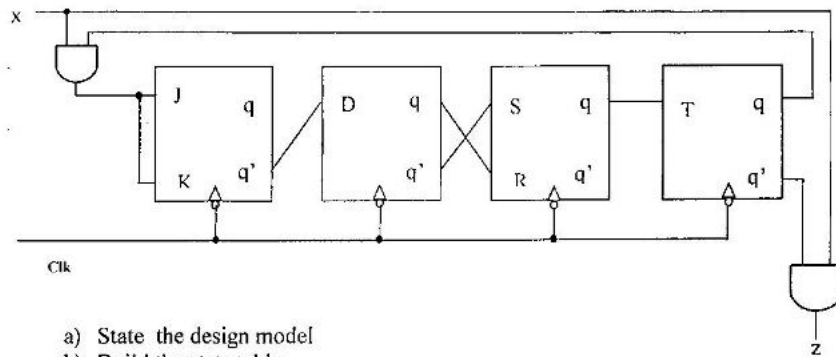

- State the design model
- Build the state table
- Given the initial state (0000) and following values for x: 110011, build the time Trace (behavior) table for q_1, q_2, q_3, q_4 and the output z.
- Use the initial state and the given values for x to complete the following time behavior diagram for the circuit.

Clk

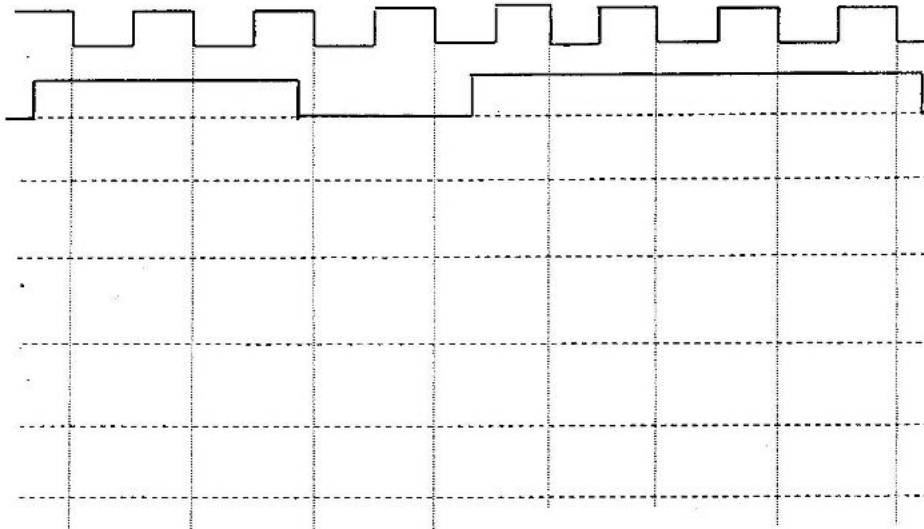

☺ Best Of LUCK ☺