



CS 504 **Digital Logic and Computer Organization**

Final Exam **5-1-2008**

Answer the Following Questions **[70 Marks]**

Question 1 **[4 marks]**

Consider the following two functions:

$$F(X,Y,Z) = XY + Z \quad , \quad G(X,Y,Z) = YZ' + X'Z$$

Draw a single logic diagram for both functions using only one (3-to-8) decoder and any gates as needed?

Question 2 **[4 marks]**

Design the full subtractor circuit using multiplexer(s) and any gates as needed? The circuit has three inputs X, Y, Z and two outputs B (output borrow) and D (Difference).

Question 3 **[4 marks]**

Draw a logic unit that perform four different logic operations using a multiplexer and any gates as needed?

Question 4 **[6 marks]**

Design the serial adder using two shift registers, a D-type flip flop and any gates as needed? Show your work.

Question 5 **[6 marks]**

Design a 3-bit binary counter using T flip flop?

Question 6 **[6 marks]**

Design a single circuit for the (3-bit) odd parity generator and checker? Use the appropriate gates and explain how the circuit works?

Question 7 **[6 marks]**

Design a (4-to-2) priority encoder with inputs D0, D1, D2, and D3. Assume that D0 has the lowest priority and D3 has the highest priority?

Question 8 **[4 marks]**

Find the essential and non essential prime implicants then simplify the following function:

$$F(A, B, C, D) = \sum m(2, 8, 9, 10, 12, 13, 14), \sum d(1, 3, 4, 5, 6, 7)$$

Question 9 **[4 marks]**

Draw the logic diagram of a 4-bit Universal Shift Register that operates as follows:

| S ₁ | S ₀ | Operation |
|----------------|----------------|---------------|
| 0 | 0 | No Change |
| 0 | 1 | Shift right |
| 1 | 0 | Shift left |
| 1 | 1 | Parallel Load |

Question 10

[10 marks]

An industrial robot that places components on a printed circuit board has **3 fail – safe sensors and an emergency shutdown switch**. The robot should keep functioning unless any of the following conditions arise:


- If the emergency switch is pressed , the system shuts down
- If sensor 1 and sensor 2 are activated at the same time, the system shuts down
- If sensor 2 and sensor 3 are activated at the same time, the system shuts down
- If all three sensors are activated at the same time then the system shuts down

- Derive the truth table for this system?
- Using K – map, obtain the minimal sum of product?
- Design the circuit using NAND gates only?
- Design the circuit using NOR gates only?
- If the time delay experienced by a NAND is 8 nanosecond and time delay experienced in a NOR is 5 nanosecond. Which implementation is faster? and by how much?

Question 11

[4 marks]


Consider the following multiplexer. What must the inputs A, B, C, D be so that the multiplexer implements the function $X = S1 S0'$?

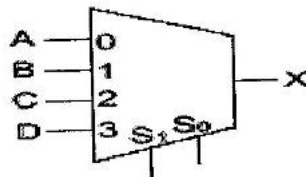

Question 12

[4 marks]


What sequence will the following counter count through?

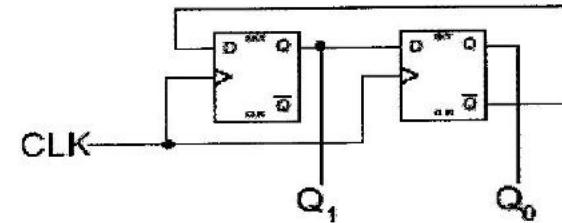

Question 13

[4 marks]

Express output function of the following figure in the simplest form?

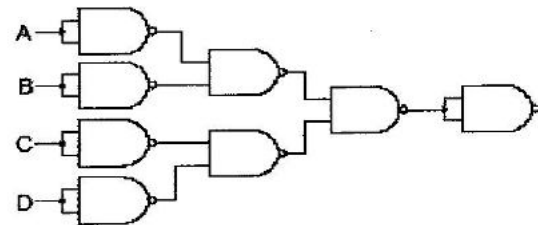

Question 14

[4 marks]

Assume that the circuit below has initially been reset. X is high and Y is low. After 4 clock pulses, What is the value of Q?

