

## Quiz No. Two

Student Name: .....

Student ID: .....

Question #	Points
1	
2	
3	
4	
Total	

## Quiz No. Two

- (1) Find all minimum expressions (sum of products and product of sums) for the following function (that is, using K-map, circle the terms on the map and write the algebraic expressions). (4.5 points)

$$F(a,b,c,d) = \sum m(0,2,4,6,10,11,15) + \sum d(8,14)$$

Start Solution Here:

F


F'


F1=

F2=

F3=

F' =

F4=

- (2) Find all minimum sum of products expression(s) for the following functions (that is, using K-map, circle the terms on the map and write the algebraic expressions). (4.5 points)

$$(a) F(a,b,c,d,e) = \sum m(0, 2, 4, 5, 12, 15, 18, 20, 22, 26, 28, 29, 30) + \sum d(8, 13, 14, 31)$$

Start Solution Here:




F1=

F2=

F3=

F4=

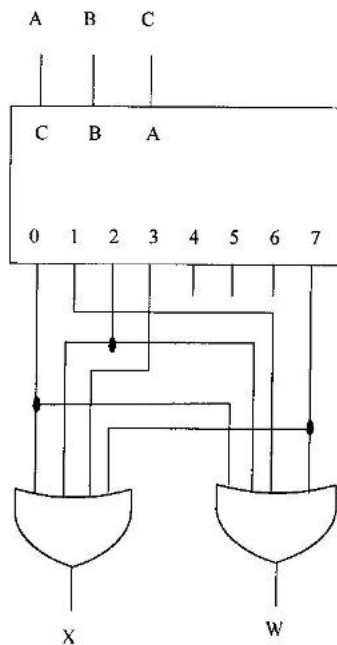- (3) Consider the following circuit with an active high output decoder.  
Draw a truth table for X and W, then extract the switching formula for the design in terms of A, B and C. (3 points)



Start Solution Here:

Truth table

A	B	C	X	W

X(a,b,c) =

W(a,b,c) =


- (4) Consider the following three functions, f, g and h of the four variables, a, b, c and d, whose minimum solutions are listed below.

$$f(a,b,c,d) = b'c'd + bc + abd$$

$$g(a,b,c,d) = c'd + b'd + b'c$$

$$h(a,b,c,d) = ac + cd' + a'c'd + bd$$

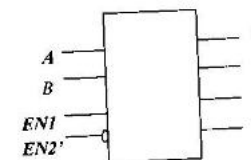Implement them using, only, decoders of the type shown (as many as needed) and three OR gates. No other gates are allowed, logic 1 and logic 0 are available. All variables are available both complemented and uncomplemented. (8 points)



EN1	EN2'	A	B	0	1	2	3
0	X	X	X	0	0	0	0
X	1	X	X	0	0	0	0
0	1	0	0	1	0	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	0	1	0
0	1	1	1	0	0	0	1

CS504

QUIZ No. 2

Start Solution Here: